

Capacitance Measurement Using Arduino

Author: Fuad Hasan, BME, KUET

1. Introduction

This project uses an Arduino board to measure the capacitance value of an unknown capacitor by calculating the charging time through a known resistor. It prints the result on the Serial Monitor either in microfarads (μF) or nanofarads (nF).

2. Key Components

- Arduino UNO (or similar)
- Capacitor (to be measured)
- Resistor (10k Ω)
- Breadboard and jumper wires
- USB Cable (for Arduino programming and serial monitoring)

3. Working Principle

1. Initialization:

The Arduino initializes pins for charging, discharging, and analog reading.

2. Charging Phase:

Arduino sets the charging pin HIGH, starting to charge the capacitor through the known resistor.

3. Timing:

A timer starts, and the code continuously reads the analog voltage across the capacitor until it reaches about 63.2% of the supply voltage (approx. 610 in 10-bit ADC scale for 5V).

4. Calculating Capacitance:

Based on the time taken to reach 63.2% charge and the known resistor value, capacitance is calculated using the formula:

$$C(\mu\text{F}) = \frac{\text{Time}(\text{ms}) \times \text{Resistance}(\Omega)}{5} \times 1000$$

5. **Displaying Results:**

The calculated capacitance is displayed on the Serial Monitor in either microfarads or nanofarads.

6. **Discharging Phase:**

Arduino stops charging, enables a discharge pin to quickly drain the capacitor, and waits until the capacitor voltage drops to zero before repeating.

4. **Circuit Overview**

- One end of the resistor is connected to 5V.
- The other end connects to one lead of the capacitor and to the analog input pin (A0).
- The other lead of the capacitor goes to Ground (GND).
- A discharge pin (Pin 9) is connected across the capacitor to speed up discharge.

5. **Code**

```
//Code written by -
```

```
//Fuad Hasan
```

```
//BME, KUET
```

```
//Initialize Pins
```

```
int analogPin = 0;
```

```
int chargePin = 8;
```

```
int dischargePin = 9; //speeds up discharging process, not necessary though
```

```
//Initialize resistor
```

```
int resistorValue = 10000;
```

```
//Initialize Timer
```

```
unsigned long startTime;
```

```
unsigned long elapsedTime;
```

```
//Initialize Capacitance Variables

float microFarads;

float nanoFarads;


void setup()
{
    pinMode(chargePin, OUTPUT);
    digitalWrite(chargePin, LOW);
    Serial.begin(9600); //Necessary to print data to serial monitor over USB

}


void loop()
{
    digitalWrite(chargePin, HIGH); //Begins charging the capacitor
    startTime = millis(); //Begins the timer

    while(analogRead(analogPin) < 610 // 648;
    {
        //Does nothing until capacitor reaches 63.25 of total voltage
    }

    unsigned long nowTime = millis();

    elapsedTime = nowTime - startTime; //Determines how much time it took to charge
    capacitor
```

```
microFarads = ((float)elapsedTime / resistorValue) * 1000;
```

```
Serial.print(elapsedTime);
```

```
Serial.print(" mS ");
```

```
if(microFarads >1) //Determines if units should be micro or nano and prints accordingly
```

```
{
```

```
    Serial.print((long)microFarads);
```

```
    Serial.println(" microFarads");
```

```
}
```

```
else
```

```
{
```

```
    nanoFarads = microFarads * 1000.0;
```

```
    Serial.print((long)nanoFarads);
```

```
    Serial.println(" nanoFarads");
```

```
    delay(500);
```

```
}
```

```
digitalWrite(chargePin, LOW); //Stops charging capacitor
```

```
pinMode(dischargePin,OUTPUT);
```

```
digitalWrite(dischargePin, LOW); //Allows capacitor to discharge
```

```
while(analogRead(analogPin) > 0)
```

```
{
```

```
    //Do nothing until capacitor is discharged
```

```
}
```

```
pinMode(dischargePin, INPUT); //Prevents capacitor from discharging
}
```

6. Code Explanation


- **Pin Initialization:**
 - analogPin = 0 -> Reads capacitor voltage.
 - chargePin = 8 -> Used to charge the capacitor.
 - dischargePin = 9 -> Used to quickly discharge the capacitor.
- **Resistor Value:**
 - 10k resistor used to control charging current.
- **Timer Variables:**
 - startTime and elapsedTime used to measure how long it takes to charge the capacitor.
- **Capacitance Calculation:**
 - Time is divided by resistance and scaled to get capacitance.
- **Charging the Capacitor:**
 - digitalWrite(chargePin, HIGH) starts charging.
 - while(analogRead(analogPin) < 610) waits until 63.2% charge.
- **Measuring and Printing:**
 - Depending on magnitude, prints either in microfarads or nanofarads.
- **Discharging the Capacitor:**
 - digitalWrite(dischargePin, LOW) discharges capacitor.
 - Waits until capacitor voltage is almost zero.

7. Conclusion

This simple Arduino-based capacitance meter provides an effective and low-cost method for measuring unknown capacitors using basic electrical principles. It offers a great introduction to both electronics and Arduino programming.

End of Document

Circuit design Mighty Gogo-Jaiks

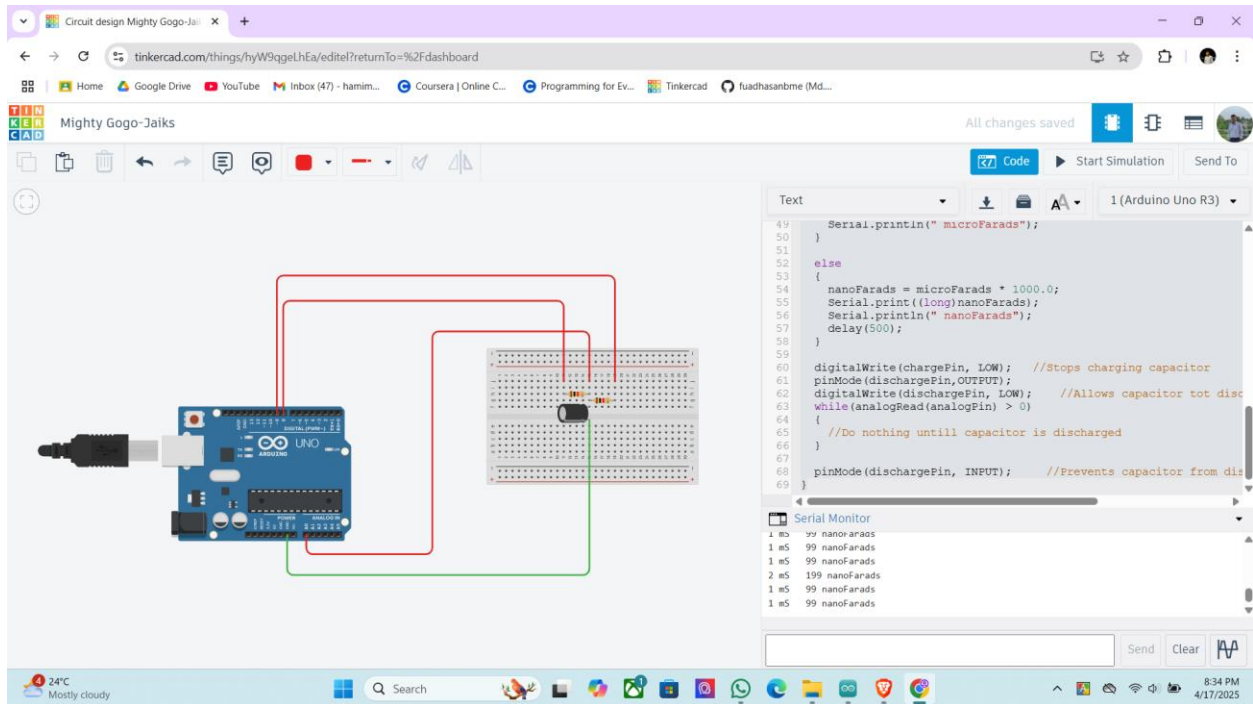

The circuit diagram shows an Arduino Uno R3 connected to a breadboard. A capacitor is connected to the breadboard. The circuit is connected to a USB Type-C cable. The code editor on the right shows a program that reads the capacitor's value and prints it to the serial monitor.

```
49 Serial.println(" microFarads");
50 }
51 else
52 {
53   nanoFarads = microFarads * 1000.0;
54   Serial.print((long) nanoFarads);
55   Serial.println(" nanoFarads");
56   delay(500);
57 }
58
59 digitalWrite(chargePin, LOW); //Stops charging capacitor
60 pinMode(dischargePin, OUTPUT);
61 digitalWrite(dischargePin, LOW); //Allows capacitor tot disc
62 while(analogRead(analogPin) > 0)
63 {
64   //Do nothing untill capacitor is discharged
65 }
66
67 pinMode(dischargePin, INPUT); //Prevents capacitor from dis
68
69 }
```

Serial Monitor

```
1 mS 99 nanoFarads
1 mS 99 nanoFarads
1 mS 99 nanoFarads
1 mS 99 nanoFarads
1 mS 99 nanoFarads
```

24°C Mostly cloudy 8:34 PM 4/17/2025